

Post-Lab Intro to Simscape

Due No due date **Points** 14 **Questions** 14 **Time Limit** None

Attempt History

	Attempt	Time	Score
LATEST	Attempt 1	89 minutes	8 out of 14 *

* Some questions not yet graded

Score for this quiz: **8** out of 14 *

Submitted Feb 18 at 8:03pm

This attempt took 89 minutes.

Question 1

1 / 1 pts

Source resistor: R1(Ω)

Correct!

80.9

Correct Answers

Between 1 and 1,000

Question 2

1 / 1 pts

Source resistor: R4 (Ω)

Correct!

80.9

Correct Answers

Between 1 and 1,000

Question 3**1 / 1 pts**Biasing resistor: R2 (Ω)**Correct!**

10

Correct Answers

Between 0 and 100

Question 4**1 / 1 pts**Biasing resistor: R3 (Ω)**Correct!**

10

Correct Answers

Between 1 and 100

Question 5**1 / 1 pts**Backflow capacitor value (in microfarads μF)**Correct!**

0.8754

Correct Answers

0 (with margin: 1)

Question 6**1 / 1 pts**

What is the current gain (amps/amps) of your amplifier?

Correct!

Correct Answers

Between 1 and 50

Question 7

1 / 1 pts

What is the voltage attenuation of your amplifier (volts/volts)?

Correct!

Correct Answers

Between 0 and 1

Question 8

Not yet graded / 1 pts

Are there any design improvements you can make to this amplifier (please list 3 or 4)?

Your Answer:

You can increase the R_{LOAD}

You can increase the resistance of R_1 and R_4

You can lower the resistances of R_2 and R_3

Question 9

1 / 1 pts

Load Resistance value: R_{load} (Ω)

Correct!

Correct Answers

4 (with margin: 0)

Question 10

Not yet graded / 1 pts

What is the function of the load resistor? Is its value significant to the performance of the amplifier? Please explain.

Your Answer:

The load resistor is added to simulate something being connected to the circuit.

The numerical value itself is not significant as an arbitrary value but would be in a real-world application.

Question 11

Not yet graded / 1 pts

Identify types of basic circuits used in the construction of this amplifier (please list 3 or 4).

Your Answer:

Resistors in series

Parallel Circuits

RC Circuit

Question 12**Not yet graded / 1 pts**

Submit your Simscape model file (both as an image and an .slx model).

 [CircuitSchematic.slx](#)

<https://sit.instructure.com/files/5828809/download>

Question 13**Not yet graded / 1 pts**

Submit plots of V_{in} , I_{in} , V_{out} , and I_{out} .

 [AllPlotsTogether.png](#)

<https://sit.instructure.com/files/5828793/download>

Question 14**Not yet graded / 1 pts**

Detail the characteristics (numerical values) of your amplifier (e.g. Source and Bias Resistors, R_{eq} , C , V_{in} , V_{out} , I_{in} , I_{out} , Current Gain, Voltage Attenuation and whatever else you think is important.)

Your Answer:

$I_{in} = 0.0183 \text{ A}$ $I_{out} = .183 \text{ A}$

$V_{in} = 3 \text{ V}$ $V_{out} = 0.63 \text{ V}$

$R_{eq} = 181.8 \text{ Ohms}$

$C = 0.8754 \text{ microfarads}$

Current Gain = 10 A/A

Voltage Attenuation = 0.21 V/V

Quiz Score: **8** out of 14